

Fri – Science

1. a. What is a battery?
 - b. Draw the symbol of a battery with 2 cells.
 - c. Draw diagrams to show the different ways of connecting 2 cells to make a battery.
2. What is an electric fuse?
3. Write the factor on which the amount of heat produced in a current carrying wire depends.
4. Write the full form of
 - a. MCB
 - b. CFL
5. Draw a circuit diagram of a closed circuit.